

# Video-39

## Controlling Multiple LEDs

This project demonstrates how to control multiple LEDs using a potentiometer and an Arduino Uno. As the potentiometer's analog value changes, different combinations of six LEDs are turned on or off to visually represent varying intensity levels. It is useful for learning analog input reading and controlling multiple digital outputs.